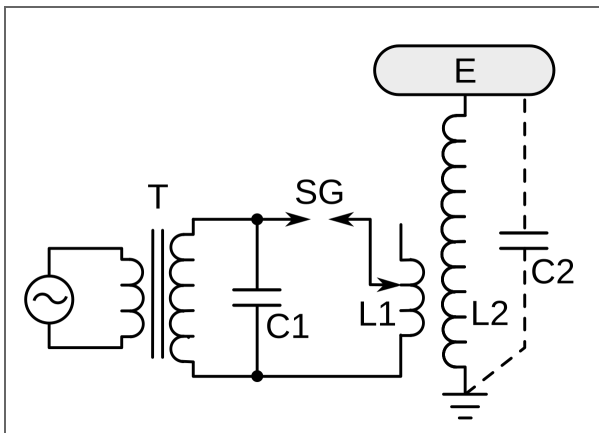


## 2.7. AC circuits & electromagnetic oscillations



### How does a Tesla coil work? ew10

- electric resonant transformer circuit
- Tesla coil with primary and secondary winding, each forming its own LC-circuit
- spark gap (SG) acts as a switch
- need to understand: **LRC-circuits, resonance, and impedance**
- **plan for today:** investigate simply AC-circuits to derive deeper understanding of R, L, and C




from **wikipedia** under **CC0 1.0 Universal**
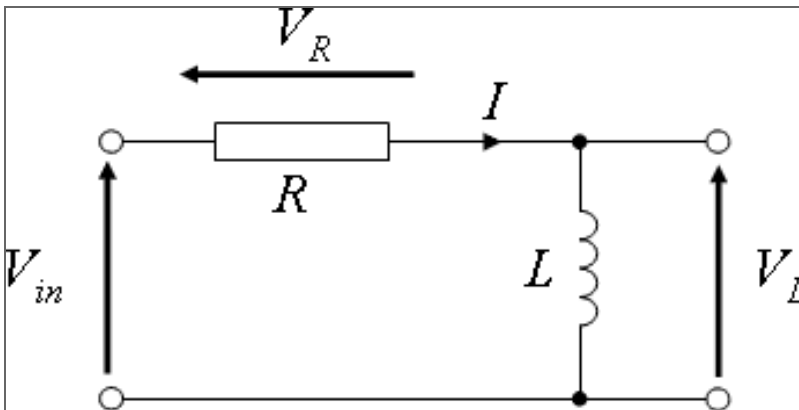
## LR-circuit

em45

- consider a simple DC circuit with the following elements in series:
  - ideal voltage source  $V_0$
  - resistor  $R$
  - inductor  $L$



from [wikipedia](#) under **CC Attribution-ShareAlike 3.0**

**Unported**

LR-circuit: Switching DC supply on

- applying Kirchhoff's loop rule gives

$$V_0 = L \frac{dI}{dt} + IR$$

- rearrange and take integral ( $0..I$  and  $0..t$ , i.e. current slowly builds up due to self-inductance):

$$\int_0^I \frac{dI}{V_0 - RI} = \int_0^t \frac{dt}{L}$$

- solving the differential equation yields

$$I(t) = \frac{V_0}{R} \left( 1 - e^{-tR/L} \right)$$

## LR-circuit: Switching DC supply on (cont')

- find  $V_L$ :

$$V_L = L \frac{dI}{dt} = \frac{d}{dt} \left( \frac{V_0}{R} (1 - e^{-tR/L}) \right)$$

$$V_L = L \left( \frac{V_0}{R} \cdot \frac{-R}{L} \cdot e^{-tR/L} \right)$$

$$V_L = -V_0 e^{-tR/L}$$

- **summary:** self-inductance causes:
  - voltage over  $L$  to be first opposed to  $V_0$  (Lenz's rule) and decaying over times
  - current building up over time

## LR-circuit: Switching DC supply off

- when the DC supply is switched off ( $V_0 = 0$ ) the inductor resists (again) change in current
- Kirchhoff's loop rule becomes

$$L \frac{dI}{dt} + IR = 0$$

- solution for decaying current is:

$$I(t) = I_0 e^{-tR/L}$$

- voltage over inductor is:


$$V_L = L \frac{dI}{dt} = \frac{d}{dt} \left( I_0 e^{-tR/L} \right) = \frac{-LR}{L} I_0 e^{-tR/L}$$

$$V_L = -V_0 e^{-tR/L}$$

LC-circuit: Fun with AC circuit

ew04

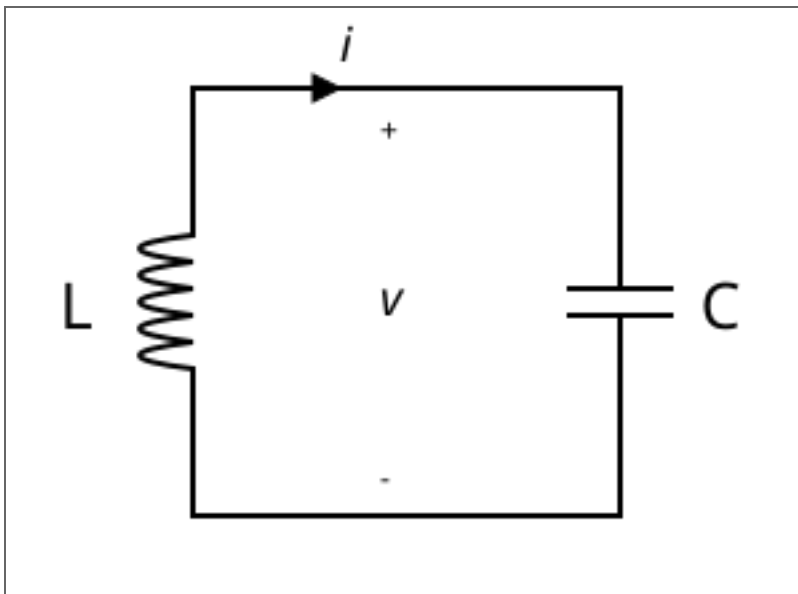**What happens if we put  $L$  and  $C$  in series in a AC circuit?**



from [wikipedia](#) under **CC Attribution-ShareAlike 3.0**

**Unported**

## LC-circuit: The equations

- applying Kirchhoff's rule leads to:

$$-L \frac{dI}{dt} + \frac{Q}{C} = 0$$

- using  $I = -\frac{dQ}{dt}$  (minus because capacitor discharges)

$$\frac{d^2Q}{dt^2} + \frac{1}{LC}Q = 0$$

- second order linear equation describing simple **harmonic oscillator** with general solution:

$$Q(t) = Q_0 \cos(\omega t + \phi) \quad \text{with the angular frequency}$$

- current  $I(t)$  is time derivative of charge:

$$I(t) = -\frac{dQ}{dt} = \omega Q_0 \sin(\omega t + \phi) = I_0 \sin(\omega t + \phi)$$

---




## LC-circuit: Electromagnetic oscillations

- the energy oscillates between capacitor (electric field) and inductor (magnetic field):

$$U = U_B + U_E = \frac{Q_0^2}{2C} \sin^2(\omega t + \phi) + \frac{Q_0^2}{2C} \cos^2(\omega t + \phi)$$

- losses are neglected

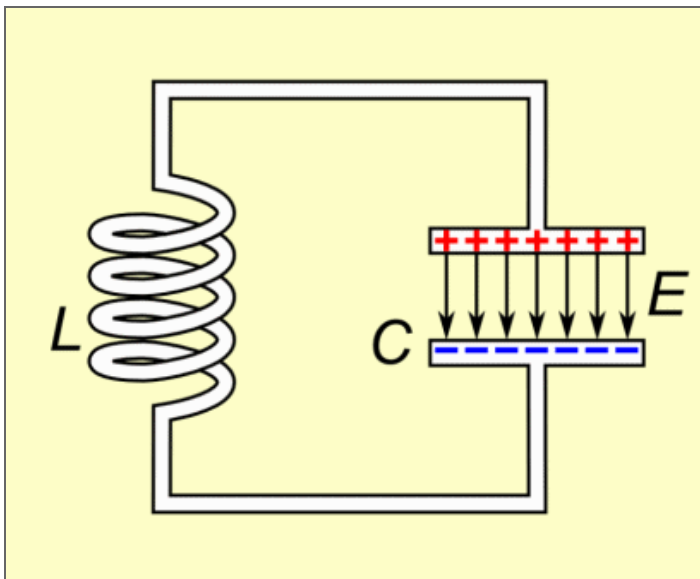


from [wikipedia](#) under [CC0 1.0 Universal](#)

---
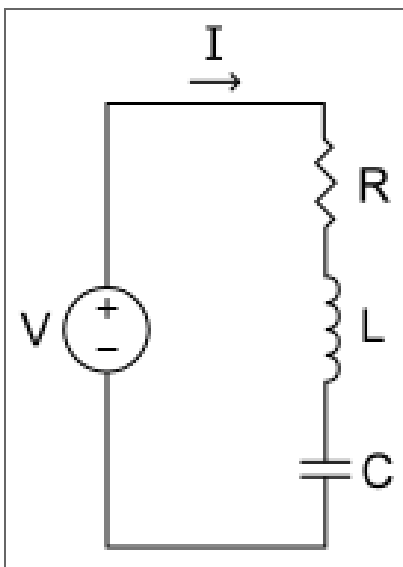
## LRC-circuit

- adding a resistor
  - introduces damping into oscillations
  - models losses



from [wikipedia](#) under **CC Attribution-ShareAlike 3.0**

**Unported**

## LRC-circuit (cont')

sim - damping LRC-circuit

- apply Kirchhoff's loop rule and use  $I = \frac{dQ}{dt}$ :

$$-L \frac{dI}{dt} - IR + \frac{Q}{C} = 0$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

- second-order linear differential equation that describes **damped harmonic oscillator**:
  - $R^2 < \frac{4L}{C}$ : Underdamped oscillation with exponential decay
  - $R^2 > \frac{4L}{C}$ : Overdamped, i.e. the damping is too strong to allow any oscillations
  - $R^2 = \frac{4L}{C}$ : Critically damped oscillation with the angular frequency

$$\omega_d = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

## Resistance vs. reactance

### ew01 - phase shift

- **LC-circuit:** energy conserved, only exchanged between  $L$  and  $C \rightarrow$  oscillation  $\rightarrow$  phase shift between  $V$  and  $I$
- **LRC-circuit:** beyond oscillation, energy dissipated as heat in  $R$
- **new concept:**
  - **resistance**  $R$  is independent of frequency and dissipates energy as heat
  - **reactance** (inductive  $X_L$  and capacitive  $X_C$ ) depends on frequency and temporarily stores energy
  - the **phase difference** between voltage and current arises due to reactance

## Resistor in AC circuit

- follows Ohm's law:  $V = IR$
- if current is sinusoidal, i.e.  $I = I_0 \cos(\omega t)$ , the voltage is:

$$V = (I_0 \cos(\omega t))R = (I_0 R) \cos(\omega t) = V_0 \cos(\omega t)$$

- $\rightarrow$  voltage and current are **in phase**
- the average power is given by

$$\bar{P} = I_{rms}^2 R$$

## Inductor in AC circuit

- the voltage across an inductor is:

$$V - L \frac{dI}{dt} = 0 \leftrightarrow V = L \frac{dI}{dt}$$

- for sinusoidal current  $I(t) = I_0 \cos(\omega t)$ , the voltage is:

$$V(t) = L \frac{d(I_0 \cos(\omega t))}{dt} = -L\omega I_0 \sin(\omega t)$$

- with  $\sin(t) = -\cos(t + \frac{\pi}{2})$

$$V(t) = \omega L I_0 \cos\left(\omega t + \frac{\pi}{2}\right) = X_L I_0 \cos\left(\omega t + \frac{\pi}{2}\right)$$

- the inductive reactance is  $X_L = \omega L = 2\pi f L$
- the **voltage leads the current by  $90^\circ$**
- since  $X_L$  **increases with frequency**, inductors resist high-frequency currents more than low-frequency ones

## Capacitor in AC circuit

- for a sinusoidal current  $I(t) = I_0 \cos(\omega t) = \frac{dQ}{dt}$ , charge at capacitor is:

$$Q(t) = \int_0^t dQ = \int_0^t I_0 \cos(\omega t) dt = \frac{I_0}{\omega} \sin(\omega t)$$

- using  $\sin \theta = \cos(\theta - \frac{\pi}{2})$ , the voltage is:

$$V(t) = \frac{Q}{C} = \frac{1}{\omega C} I_0 \sin(\omega t) = \frac{I_0}{\omega C} \cos\left(\omega t - \frac{\pi}{2}\right) =$$

- the capacitive reactance is  $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$
  - the **voltage lags the current by  $90^\circ$**
  - since  $X_C$  **decreases with frequency**, capacitors resist low-frequency currents more than high-frequency ones
-

## Summary of AC circuit components

- resistor:
  - no phase shift
  - dissipates energy as heat
- inductor:
  - voltage leads current
  - reactance  $X_L = \omega L$
- capacitor:
  - voltage lags current
  - reactance  $X_C = \frac{1}{\omega C}$



# Impedance

- impedance determines the relationship between voltage and current in AC circuits
- impedance combines resistance and reactance into a complex quantity:

$$Z = R + j(X_L - X_C)$$

- its magnitude is  $Z = \sqrt{R^2 + (X_L - X_C)^2}$  and its phase angle is  $\tan \phi = \frac{X_L - X_C}{R}$
- impedance in series:  $Z_{net} = \sum_i Z_i$
- impedance in parallel:  $\frac{1}{Z_{net}} = \sum_i \frac{1}{Z_i}$

## Revisiting AC LRC-circuit: Phasor diagrams

### sim - Phasor diagram

- in a series LRC-circuit the sum of the voltage drops equals the source voltage:

$$V = V_R + V_L + V_C$$

- in the phasor diagram:
  - $V_R$  is drawn along the positive x-axis (in phase with the current)
  - $V_L$  is drawn  $90^\circ$  ahead of  $V_R$
  - $V_C$  is drawn  $90^\circ$  behind  $V_R$
- the resultant voltage is found by vector addition:

$$V_0 = I_0 Z \quad \text{with} \quad Z = \sqrt{R^2 + (X_L - X_C)^2}$$

# Impedance matching

e135 - CASSY

- maximum power transfer occurs when the source impedance matches the load impedance:

$$Z_1 = Z_2$$

- for purely resistive circuits, maximum power is delivered when  $R_{\text{source}} = R_{\text{load}}$
- mismatched impedances lead to reduced power transfer efficiency and potential signal distortion

## Revisiting AC LRC-circuit: Resonance

### sim - Resonance

- resonance occurs when the inductive and capacitive reactances cancel:  $X_L = X_C$
- the impedance is purely resistive:

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = R$$

- $\rightarrow$  the resonant (angular) frequency is




$$\omega_0 = \sqrt{\frac{1}{LC}} \leftrightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

- $\rightarrow$  voltage and current are in phase:  $\phi = 0$
- shape of resonance curve depends on the value of  $R$

# Filters

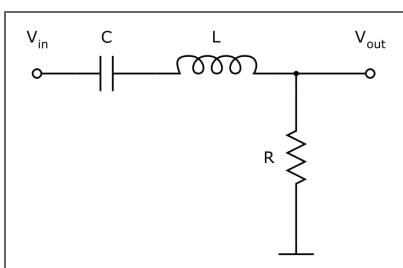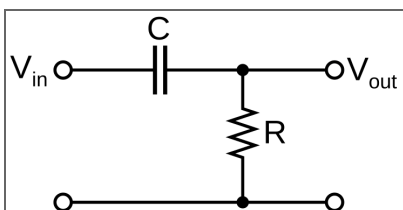
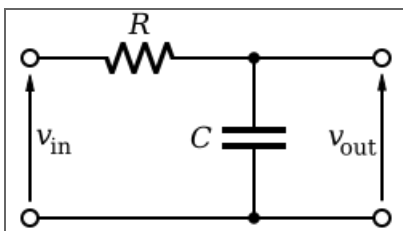
## ew07 - high/low pass

- low-pass filters allow low-frequency signals to pass while attenuating high-frequency ones
- high-pass filters allow high-frequency signals to pass while attenuating low-frequency ones
- band-pass filters allow frequency band to pass while attenuating frequencies below and above the band
- these filters are common in signal processing and audio electronics



*[left] from **wikipedia**, public domain; [middle] from **wikipedia** under **CC Attribution-ShareAlike 4.0 International**; [right] from **wikipedia**, public domain*

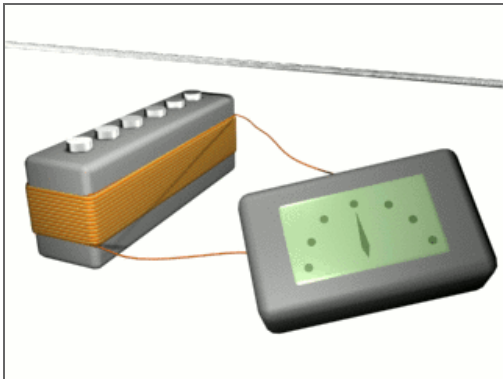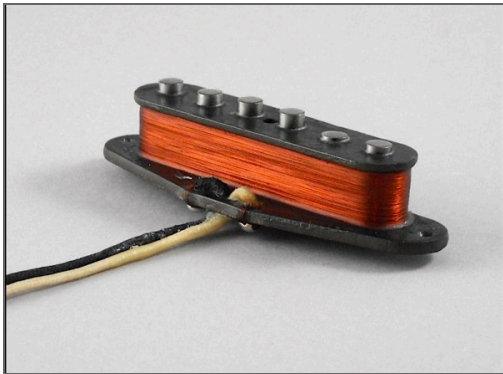Demo induction, electromagnets, filters, and resonance



*[left] from [wikipedia](#) under [CC Attribution-ShareAlike 4.0 International](#) [right] from [wikipedia](#) under [CC Attribution-ShareAlike 3.0 Unported](#)*  
**YouTube - bandpass filter in action**